

Simulate on Proteus:

1. (Make one schematic for the entire problem)
  - a) Take a number from 0 to 255 (8 bit) using logic-states and count the number of 1 bits using a **counter**.
  - b) Count the number of 1 bits at odd positions using a **counter**. (Indexing starts from 0 at LSB)

Example-  $(11111110)_2 == (254)_{10}$

Number of 1 bits=7

Number of 1 bits at odd position=4 (1,3,5,7)

2. Take a 7 bit number from 5-127 and add 5 to it in one clock cycle and divide by 2 in the next clock cycle alternately until it becomes 5.  
**Count the number of clock cycles it took to become 5 using a counter and display the output as logic probes.**
3. A 2732 ROM has an array of 5 numbers,  $0 \leq \text{each number} \leq 15$ . Find the **sum** of all the numbers and display the output as logic probes.  
Run the python file to get the Ass\_2.bin file or directly use the Ass\_2.bin file given.  
[Download Link](#)  
Given array:- [10,2,9,3,15]

PCB Design Problem (ONLY FOR DIGISIM):

4. Implement the PCB design for a **full adder** (*1 bit for 1st yearites and 2 bit for 2nd yearites*)  
The PCB components selected should be of surface mount type.  
U are free to use any company or ic number of the components , however sparkfun is recommended  
PCB should have 2 layers top and bottom  
Using Autorouter is allowed  
U are also required to write ur name on the PCB

**Take the screenshots of the schematic , board and Gerber file and upload them as well as the files on a folder in your drive or github repo. Submit the drive link/github repo in the form with view access to everyone.**